



Roll No:

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

B.TECH
(SEM I) THEORY EXAMINATION 2020-21
BASIC OF ELECTRICAL ENGINEERING

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A


1. Attempt all questions in brief.

2 x 10 = 20

| Qno. | Question | Marks | CO |
|------|---|-------|----|
| a. | Define ideal voltage and current source. | 2 | 1 |
| b. | Define Active and Passive Elements. | 2 | 1 |
| c. | Define Form factor and Peak Factor. | 2 | 2 |
| d. | Classify the losses in transformer. | 2 | 3 |
| e. | Explain True power, reactive power and Apparent power | 2 | 3 |
| f. | What is meant by the term speed regulation | 2 | 4 |
| g. | Why transformer is not used on DC | 2 | 4 |
| h. | Define the term slip | 2 | 4 |
| i. | Write down the application of Synchronous Motor. | 2 | 4 |
| j. | Write application of Single Phase Induction Motor. | 2 | 4 |

SECTION B

2. Attempt any three of the following:
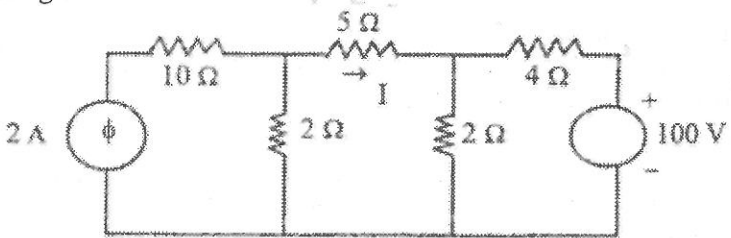
| Qno. | Question | Marks | CO |
|------|--|-------|----|
| a. | Apply mesh analysis , obtain the current through 5 ohm resistance in the following circuit  | 10 | 1 |
| b. | Obtain equivalent Star from Delta in Star-Delta Transformation | 10 | 1 |
| c. | Derive expression for average value and RMS value of Half wave rectifier voltage output. | 10 | 2 |
| d. | Why Single Phase induction motor is not self starting. What are different methods to make self starting. Explain one of them | 10 | 3 |
| e. | A balanced star connected load of $(6+j8)$ ohm per phase connected to a balance 3 phase, 400V supply. Find the line current, power factor, power and total volt-amperes. | 10 | 3 |

SECTION C

3. Attempt any one part of the following:

| Qno. | Question | Marks | CO |
|------|---|-------|----|
| a. | Show the condition for resonance in a parallel R-L-C circuit. State the application of series. | 10 | 2 |
| b. | If load draws a current of 10A at 0.8 p.f lagging, when connected to 100 volt supply, calculate the values of real, reactive and apparent powers. And also find the resistance of load. | 10 | 2 |



Roll No:

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

4. Attempt any one part of the following:

| Qno. | Question | Marks | CO |
|------|--|-------|----|
| a. | <p>Using Thevenin Theorem , Determine the current through 6 ohm</p> | 10 | 1 |
| b. | <p>Find the equivalent resistance of the following circuit and calculate the current supplied by source.</p> | 10 | 1 |

5. Attempt any one part of the following:

| | | | |
|----|--|----|---|
| a. | Derive the Emf equation of single phase transformer. A single phase 100KVA, 6.6kV/230 V, 50 Hz, transformer has 90% efficiency at 0.8 Lagging power factor both at full load and also at half load. Determine iron and copper loss at full load for transformer. | 10 | 3 |
| b. | Derive the relationship between line current, Phase current, line voltage and phase voltage in a 3-phase star-connected and delta connected circuits. | 10 | 3 |

6. Attempt any one part of the following:

| | | | |
|----|---|----|---|
| a. | A 4-Pole , 3 phase induction motor runs at 1440 rpm. Supply voltage is 500 V at 50 Hz. Mechanical power output is 20.3 Hp and mechanical loss is 2.23 Hp. Calculate: (i) Mechanical Power Developed (ii) Rotor Cu Loss (iii) Efficiency | 10 | 4 |
| b. | Draw and explain the Torque-Slip Characteristics of Three Phase Induction Motor. | 10 | 4 |

7. Attempt any one part of the following:

| | | | |
|----|---|----|---|
| a. | Explain (i) MCB (ii) ELCB (iii) MCCB | 10 | 5 |
| b. | Explain different types of Wires and Cables. | 10 | 5 |