

Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--


**BTECH**  
**(SEM I) THEORY EXAMINATION 2021-22**  
**EMERGING DOMAIN IN ELECTRONICS ENGINEERING**

**Time: 3 Hours****Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**

- a. Determine  $\beta$ , if  $I_E = 5 \text{ mA}$ ,  $I_C = 4.95 \text{ mA}$ .
- b. Define transconductance of JFET.
- c. What do you mean by CMRR?
- d. Differentiate the BJT and JFET.
- e.  $(1010110100.110)_2 = (\ )_{16}$ ?
- f. Differentiate between Avalanche and Zener breakdown.
- g. Simplify the Boolean function using Boolean Algebra theorems:  
 $A B C' + A B C' + A B C' + A B C'$
- h. Differentiate between Microprocessor and Microcontroller.
- i. What is Doping? What is the need of Doping?
- j. What is RADAR? Write down two applications of RADAR.

**SECTION B****2. Attempt any three of the following: 10 x 3 = 30**

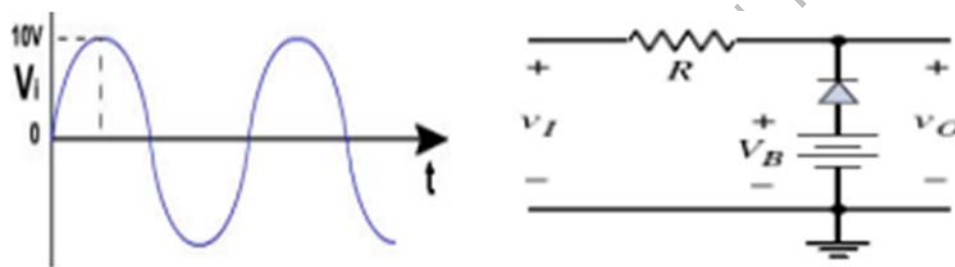- a. What do mean by clipper? Draw the output waveform of the given circuit.



- b. Draw the Structure of Depletion type N-MOSFET. Explain its operation with characteristic graph.
- c.
  - i) Subtract using 10's complement:  $(9754)_{10} - (364)_{10}$
  - ii) Subtract using 1's complement:  $(10111)_2 - (110011)_2$
- d. Describe AM modulation and Demodulation technique with adequate diagram.
- e. Write down the characteristics of ideal OP-AMP. Derive the expression for gain of OP-AMP as non-inverting amplifier.

**SECTION C****3. Attempt any one part of the following: 10 x 1 = 10**


- (a) Define Voltage Multiplier. Draw the circuit and explain the working of voltage Tripler and Quadrupler circuit.
- (b) Draw the V-I characteristics of zener diode. Determine the network of figure given below, determine the range of  $V_{in}$  that will maintain  $V_L$  at 8V and not

Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2021-22**  
**EMERGING DOMAIN IN ELECTRONICS ENGINEERING**

exceeded the maximum power rating of the Zener diode.

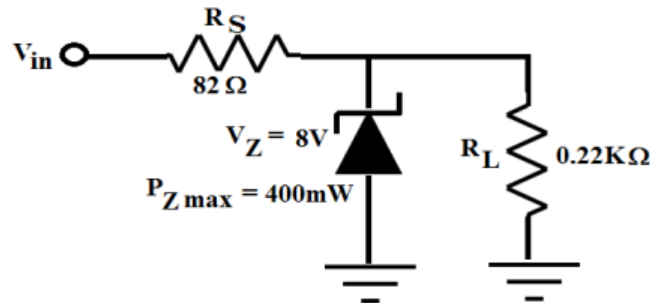


4. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Describe the construction and working of a NPN transistor in CE configuration with respect to size and doping. Also, draw the input and output characteristic graph.
- (b) Define  $\alpha$  and  $\beta$  with respect to BJT and derive the relationship between them. A transistor having  $\alpha = 0.975$  and reverse saturation current  $I_{CBO} = 10\mu A$  is operated in CE mode. If the base current is  $250\mu A$ . Calculate  $I_E$  and  $I_C$ .

5. Attempt any *one* part of the following: 10 x 1 = 10

- (a) (i) Draw and explain the working of Integrator and Differentiator using OP-AMP.  
(ii) Write Short note on basic elements of communication system.
- (b) (i) Determine the output voltage of an OPAMP for the input voltage of  $V_1 = 150\mu V$  and  $V_2 = 140\mu V$ . The amplifier has differential gain  $A_d = 4000$  and CMRR is 100.  
(ii) Determine the output of the following circuit.  
Given  $V_1 = V_2 = 0.15V$

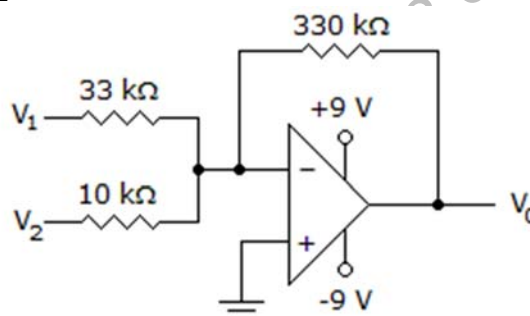

6. Attempt any *one* part of the following: 10 x 1 = 10

- (a) i) Describe briefly Satellite Communication.  
ii) Explain Positive and Negative Clamper using suitable circuit diagram and input/output waveform.
- (b) An audio frequency signal  $5\sin(2\pi \times 500t)$  is used to amplitude modulate a carrier of  $25\sin(2\pi \times 10^5 t)$ . Calculate:  
(i) Modulation index  
(ii) Amplitude of Each side band

Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2021-22**  
**EMERGING DOMAIN IN ELECTRONICS ENGINEERING**

---

- (iii) Total power
- (iv) Bandwidth
- (v) Transmission efficiency

7. Attempt any *one* part of the following: **10 x 1 = 10**

- (a) Minimize using K-map and realize using NOR gates only.  $F(A, B, C, D) = \Pi M(3, 4, 5, 7, 9, 13, 14, 15)$ .  $d(0, 2, 8)$ .
- (b)  $F(A, B, C, D, E) = \Sigma m(0, 1, 2, 4, 5, 6, 10, 13, 14, 18, 21, 22, 24, 26, 29, 30)$ . Simplify the function with help of K-map and realize the simplified function using basic logic gates.

QP22P2\_290

| 25-Mar-2022 08:59:55 | 117.55.242.131